


# Electric Current

Submitted by: I.D. 039622568

## The problem:

Given the values:  $\varepsilon_1 = 1\text{ V}$ ,  $\varepsilon_2 = 0.5\text{ V}$ ,  $\varepsilon_3 = 0.6\text{ V}$ ,  $R_1 = R_2 = 0.5\ \Omega$ ,  $R_3 = 1\ \Omega$ ,  $R_4 = 0.4\ \Omega$ ,  $R_5 = R_6 = 0.6\ \Omega$ ,  $R_7 = 0.7\ \Omega$

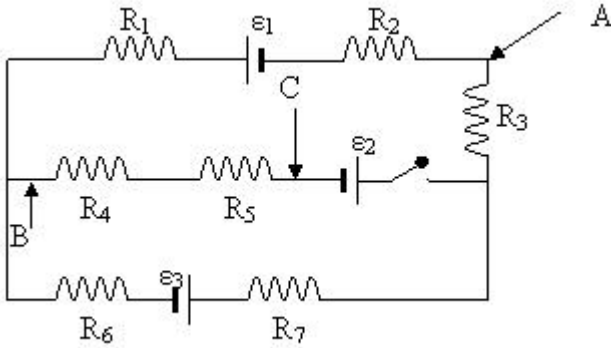1. Calculate the current flowing through each resistor, and the potential difference between B and A when the switch is open.
2. Calculate the current flowing through each resistor, and the potential difference between B and C when the switch is closed.



## The solution:

1. Since the switch is open we can disregard the middle branch of the circuit, leaving only a circuit with resistors and voltage sources in series. By using Ohm's Law we find:

$$V_t = \varepsilon_1 + \varepsilon_3 = 1 + 0.6 = 1.6\text{ V} \quad (1)$$

$$R_t = R_1 + R_2 + R_3 + R_6 + R_7 = 0.5 + 0.5 + 1 + 0.6 + 0.7 = 3.3\ \Omega \quad (2)$$

$$I = \frac{V_t}{R_t} = \frac{\varepsilon_1 + \varepsilon_3}{R_1 + R_2 + R_3 + R_6 + R_7} = \frac{1.6}{3.3} = 0.485\text{ A} \quad (3)$$

With the current moving counter clockwise because of the direction of the voltage sources.

Now in order to calculate the potential difference between B and A, all we have to do is calculate the voltage between these points:

$$V_{BA} = \varepsilon_1 - I(R_1 + R_2) = 1 - I = 0.515\text{ V} \quad (4)$$

2. Now that the switch is closed we can no longer disregard the middle branch, and we have to use Kirchhoff's laws.

We will choose the right node as our junction and assume that  $I_1$  comes from above,  $I_2$  from below and  $I_3$  flows to the left.

Now, our first path will be clockwise through  $R_1, \varepsilon_1, R_2, R_3, \varepsilon_2, R_5, R_4$ , and our second will be likewise clockwise through  $R_1, \varepsilon_1, R_2, R_3, R_7, \varepsilon_3, R_6$ . giving us the following equations:

$$I_1 + I_2 = I_3 \quad (5)$$

$$I_1 R_1 + \varepsilon_1 + I_1 R_2 + I_1 R_3 + \varepsilon_2 + I_3 R_5 + I_3 R_4 = 0 \quad (6)$$

$$I_1 R_1 + \varepsilon_1 + I_1 R_2 + I_1 R_3 - I_2 R_7 + \varepsilon_3 - I_2 R_6 = 0 \quad (7)$$

Using simple math, we found the currents:  $I_1 = -0.6 A$ ,  $I_2 = 0.3 A$  and  $I_3 = -0.3 A$ , while the negative sign signals that the direction in which these currents flow is opposite to the one we chose. in order to find the potential difference between points B and C we calculate the voltage, keeping in mind that  $I_3$  now has a new direction. thus:

$$V_{BC} = I_3(R_4 + R_5) = 0.3(0.4 + 0.6) = 0.3 V \quad (8)$$